

Ohm's Law and Resistance in circuits

1. Measurements of the p.d. across a resistor and the current in the resistor give the following results.


$$\begin{aligned} \text{p.d.} &= (30.00 \pm 0.03) \text{ V} \\ \text{current} &= (2.00 \pm 0.01) \text{ A} \end{aligned}$$

Use these results to calculate the resistance of the resistor and express your answer in the form

resistance \pm uncertainty


6

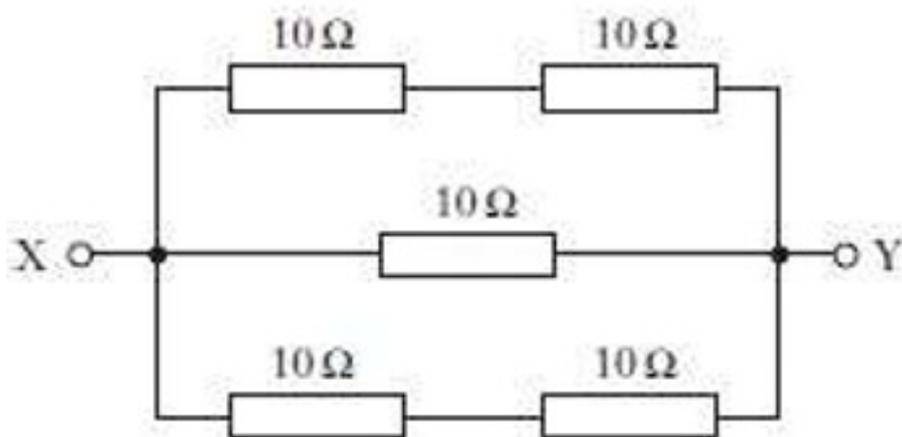2. The diagram shows part of an electrical circuit.



What is the resistance between X and Y?


3 Five resistors are connected as shown.

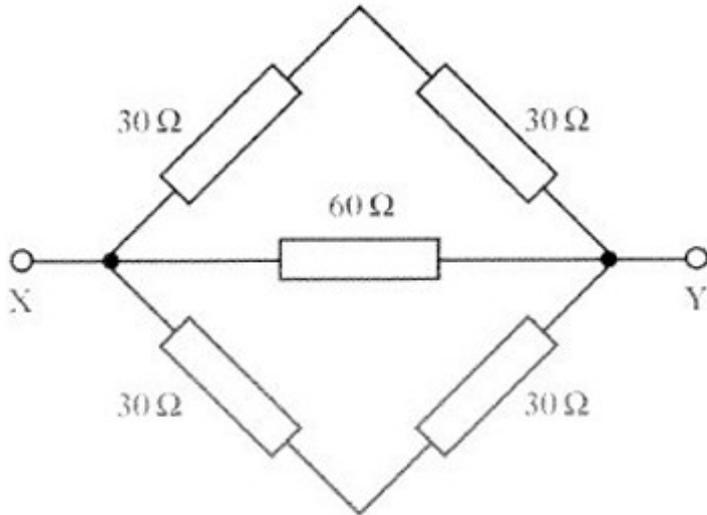

The resistance between X and Y is

2

4 A circuit is set up as shown.

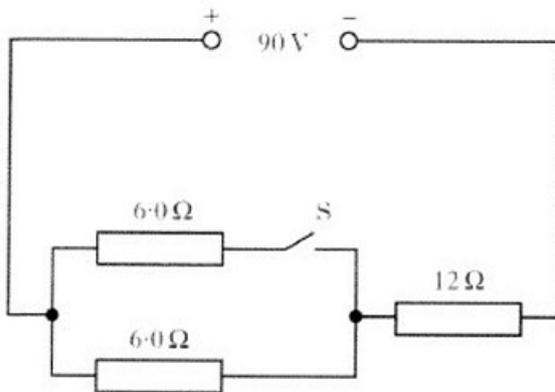

The internal resistance of the supply is negligible.


Which row in the table shows the potential difference (p.d.) across the $12\ \Omega$ resistor when switch S is open and when S is closed?

	<i>p.d. across $12\ \Omega$ resistor when S is open/V</i>	<i>p.d. across $12\ \Omega$ resistor when S is closed/V</i>
A	30	18
B	45	45
C	60	45
D	60	72
E	72	60

2

Potential Dividers and Wheatstone Bridges

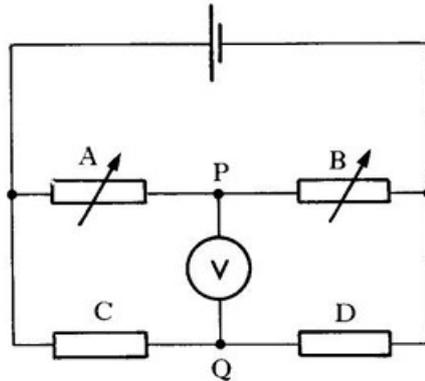- 5 Two potential dividers are connected in parallel to form the Wheatstone bridge circuit shown below.




The reading on the voltmeter is 0 V.

Describe how the resistances of A, B, C and D are related.

1


6. The following circuit is set up.

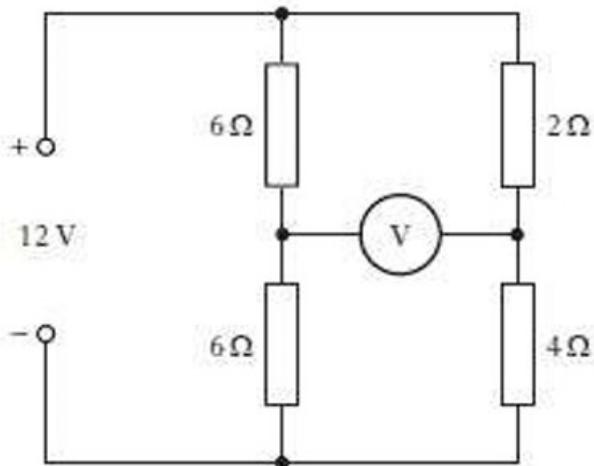

What is the reading on the voltmeter?

3

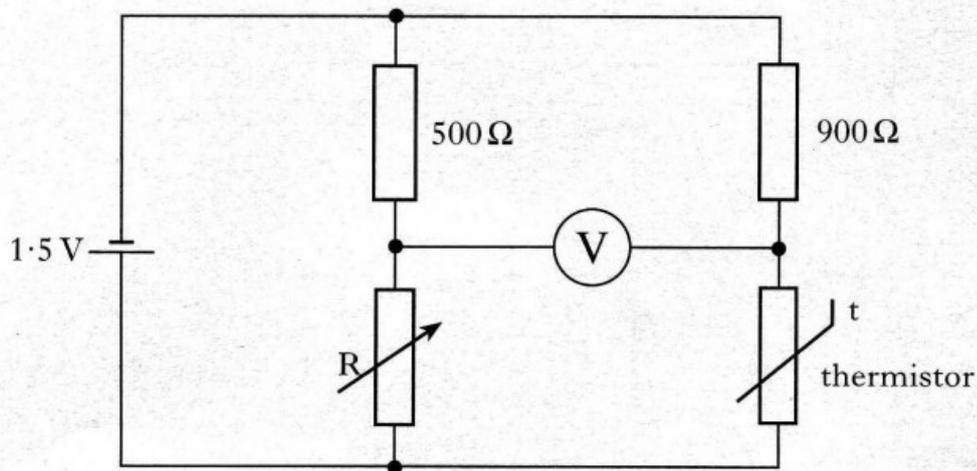- 7 A pupil uses a Wheatstone bridge to investigate how the resistance of a thermistor is affected by its temperature. The circuit is shown below.



- (a) The thermistor is placed in water at a temperature of 20°C and the resistance of the variable resistor, R , is adjusted to $450\ \Omega$ to balance the bridge.

Calculate the resistance of the thermistor at this temperature.

2

- (b) Several pupils use the circuit to find the resistance of the thermistor when the water temperature is 30°C . The values they obtain are as follows.

852 Ω 854 Ω 848 Ω 851 Ω 853 Ω

Calculate:

- i) The **mean** of the values.

1

- ii) The **random uncertainty** in the **mean**.

1


- (c) Their teacher says that there may have been a systematic uncertainty in the investigation.

Describe what is meant by a **systematic uncertainty**.

1

8

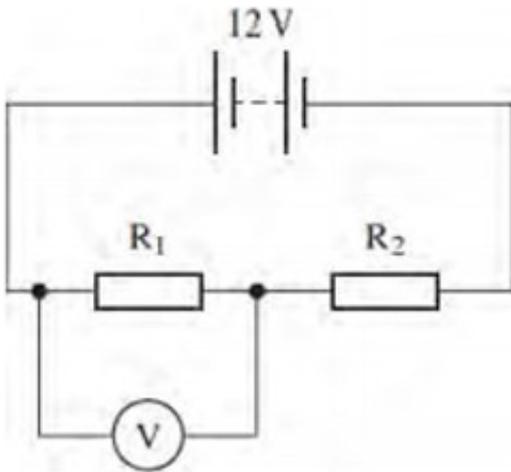The figure below shows two resistors, R_1 and R_2 , connected in series with a battery of emf 12 V and negligible internal resistance.



(a) The reading on the voltmeter is 8.0 V and the resistance of R_2 is 60 Ω .

(i) Calculate the current in the circuit.

answer = A

(2)

(ii) Calculate the resistance of R_1 .

answer = Ω

(1)

(iii) Calculate the charge passing through the battery in 2.0 minutes. Give an appropriate unit for your answer.

answer = unit =

(2)

(b) In the circuit shown in the figure above R_2 is replaced with a thermistor. State and explain what will happen to the reading on the voltmeter as the temperature of the thermistor increases.

.....

.....

.....

.....

.....

.....

(3)

(Total 8 marks)